

CSE 125 Lab 1: Behavioral Verilog


Date: 04/12/2020

Name: Zhongming Liao, Chuanshi Zhu

Lab Group: 20

1. Linear Feedback Shift Register

a. Screenshot

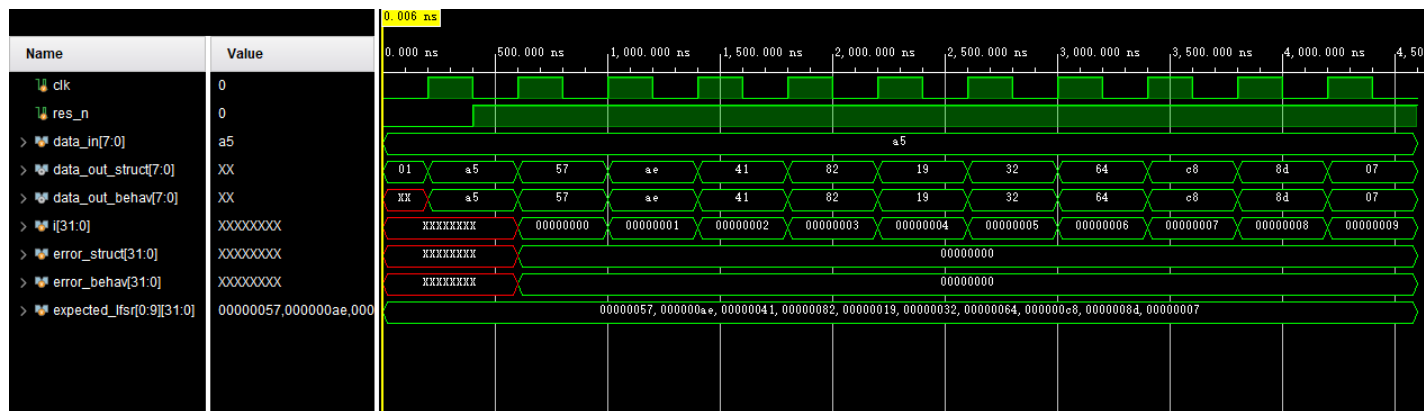

b. Result

10 outputs:

data_out_struct[7:0]: a5, 57, ae, 41, 82, 19, 32, 64, c8, 8d;

data_out_behav[7:0]: a5, 57, ae, 41, 82, 19, 32, 64, c8, 8d;

lfsr_structural:

resource:

wns = -0.155ns, target clock period = 20ns

Fmax:

$$F_{max} = 1/(20 - (-0.155)) = 1/20.155 = 0.05\text{Mhz}$$

lfsr_behavioural:

resource:


wns = -0.58ns, target clock period = 20ns

Fmax:

$$F_{max} = 1/(20 - (-0.58)) = 1/20.58 = 0.049\text{Mhz}$$

2. Build a Multiplier using an Accumulator

a. Screenshot

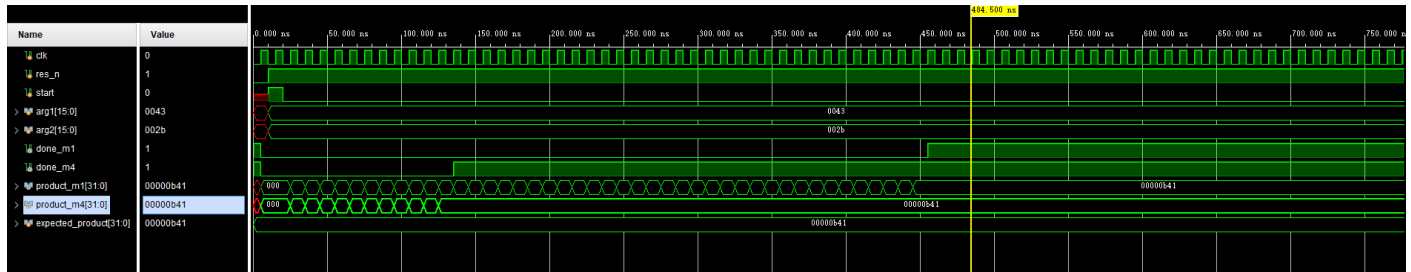


b. Result

Multiplier_1:

LUT and FF:

Resource	Utilization	Available	Utilization%
LUT	52	41000	0.13
FF	65	82000	0.08
IO	68	300	22.67

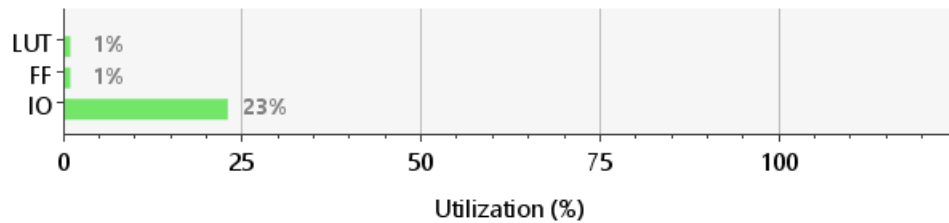

Fmax:

wns = -0.466ns


target clock period: 11ns

$F_{max} = 1/(11+0.466) = 0.0872\text{Mhz}$

multiplier_4:

LUT and FF:

Resource	Utilization	Available	Utilization%
LUT	187	41000	0.46
FF	63	82000	0.08
IO	68	300	22.67

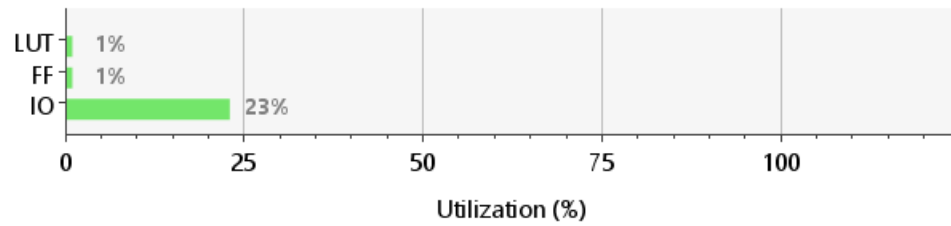

Fmax:

wns = -3.823ns

target clock period: 11ns

$F_{max} = 1/(11+3.823) = 0.0675\text{Mhz}$